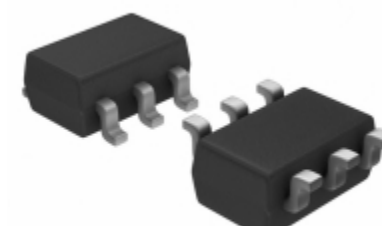


| AOZ1083CI           |   |
|---------------------|---|
| Numéro d'article    | <a href="#">AOZ1083CI</a>   |
| Fabricant           | <a href="#">Alpha and Omega Semiconductor, Inc.</a>   |
| La description      | IC LED DRIVER RGLTR DIM SOT23-6   |
| Quantité disponible | 6000 pcs in stock   |
| Feuilles de données | <a href="#">AOZ1083CI.pdf</a>   |
| AOZ1083CI Price     | <a href="#">Demande de prix et délai de livraison en ligne</a><br>or Email us: <a href="mailto:Info@ariat-tech.com">Info@ariat-tech.com</a> |


[OBTENIR UN DEVIS](#)

| Informations techniques de AOZ1083CI |   |                                |  |
|--------------------------------------|---|--------------------------------|--|
| Référence fabricant                  | <a href="#">AOZ1083CI</a>                           | Catégorie                      | <a href="#">Circuits intégrés (CI)</a> |
| Fabricant                            | <a href="#">Alpha and Omega Semiconductor, Inc.</a> | La description                 | IC LED DRIVER RGLTR DIM SOT23-6        |
| Paquet / cas                         | Tape & Reel (TR)                                    | Quantité disponible            | 6000                                   |
| Séries                               | EZBuck™   | La fréquence                   | 1.5MHz                                 |
| Température de fonctionnement        | -40 °C ~ 85 °C (TA)                                 | Type de montage                | Surface Mount                          |
| Type                                 | DC DC Regulator                                     | Applications                   | Lighting                               |
| Package / Boîte                      | SOT-23-6  | Package composant fournisseur  | SOT-23-6                               |
| Commutateur (s) interne              | Yes   | Tension - Sortie               | -                                      |
| Courant - Sortie / Canal             | 1.2A  | Nombre de sorties              | 1                                      |
| topologie                            | Step-Down (Buck)                                    | Alimentation en tension (max.) | 26V                                    |
| Alimentation en tension (Min)        | 3V  | Atténuation                    | PWM                                    |
| Emballage                            | Tape & Reel (TR)                                    |                                |  |

AOZ1083CI 6000 pcs Nouveau et original en stock, Trouver AOZ1083CI Stock, Fiche technique, PDF, Inventaire au format Ariat-Tech.com en ligne, commandez AOZ1083CI Alpha and Omega Semiconductor, Inc. avec garantie et confiance. RFQ AOZ1083CI: [Info@Ariat-Tech.com](mailto:Info@Ariat-Tech.com)

| Pièces connexes AOZ1083CI |                               |  |                                     |           |
|---------------------------|-------------------------------|--|-------------------------------------|-----------|
| Image                     | Numéro d'article              | La description                             | Fabricant                           | Qté       |
|                           | <a href="#">AOZ1117TI-15L</a> | AOZ1117TI-15L ALPHA                        | ALPHA                               | 15000 pcs |
|                           | <a href="#">AOZ1073AIL_2</a>  | IC REGULATOR BUCK SOIC                     | Alpha and Omega Semiconductor, Inc. | 500 pcs   |
|                           | <a href="#">AOZ1075AI</a>     | AOZ1075AI AOS                              | AOS                                 | 12232 pcs |
|                           | <a href="#">AOZ1073AIL_6</a>  | IC REGULATOR BUCK SOIC                     | Alpha and Omega Semiconductor, Inc. | 500 pcs   |
|                           | <a href="#">AOZ1075HAI</a>    | IC REGULATOR BUCK SOIC                     | Alpha and Omega Semiconductor, Inc. | 500 pcs   |
|                           | <a href="#">AOZ1096PI</a>     | AOZ1096PI AOS                              | AOS                                 | 3108 pcs  |
|                           | <a href="#">AOZ1081AI</a>     | IC LED DRIVER RGLTR DIM 1.8A 8SO           | Alpha and Omega Semiconductor, Inc. | 1800 pcs  |
|                           | <a href="#">AOZ1076PI</a>     | AOZ1076PI AOS                              | AOS                                 | 12000 pcs |
|                           | <a href="#">AOZ1079PI</a>     | AOZ1079PI AOS                              | AOS                                 | 9000 pcs  |
|                           | <a href="#">AOZ1094AIL</a>    | IC REG BUCK ADJ 5A 8SOIC                   | Alpha and Omega Semiconductor, Inc. | 1344 pcs  |
|                           | <a href="#">AOZ1110QI</a>     | IC REG BUCK ADJ 4A SYNC 24QFN              | Alpha and Omega Semiconductor, Inc. | 500 pcs   |
|                           | <a href="#">AOZ1092DI</a>     | IC REG BUCK ADJ 3A 8DFN                    | Alpha and Omega Semiconductor, Inc. | 601 pcs   |
|                           | <a href="#">AOZ1092DIL</a>    | IC REGULATOR BUCK DFN                      | Alpha and Omega Semiconductor, Inc. | 500 pcs   |
|                           | <a href="#">AOZ1075AI_2</a>   | IC REGULATOR BUCK SOIC                     | Alpha and Omega Semiconductor, Inc. | 500 pcs   |
|                           | <a href="#">AOZ1073AIL_8</a>  | IC REGULATOR BUCK SOIC                     | Alpha and Omega Semiconductor, Inc. | 500 pcs   |
|                           | <a href="#">AOZ1094AI</a>     | AOZ1094AI Alpha & Omega Semiconductor Inc. | Alpha and Omega Semiconductor, Inc. | 12226 pcs |
|                           | <a href="#">AOZ1094AIL_2</a>  | IC REG BUCK 8SOIC                          | Alpha and Omega Semiconductor, Inc. | 500 pcs   |
|                           | <a href="#">AOZ1073AIL_3</a>  | IC REGULATOR BUCK SOIC                     | Alpha and Omega Semiconductor, Inc. | 500 pcs   |
|                           | <a href="#">AOZ1094DIL</a>    | IC REG BUCK ADJ 5A 8DFN                    | Alpha and Omega Semiconductor, Inc. | 88999 pcs |
|                           | <a href="#">AOZ1084DI</a>     | IC LED DRVR RGLTR DIM 1.2A 8DFN            | Alpha and Omega Semiconductor, Inc. | 1080 pcs  |

**IC Chips & IGBT Module - Numéro de pièce en stock à chaud**

|                                |                               |                               |                               |                               |
|--------------------------------|-------------------------------|-------------------------------|-------------------------------|-------------------------------|
| <a href="#">AOZ1038DI</a>      | <a href="#">AOZ1038DI-1</a>   | <a href="#">AOZ1039DI</a>     | <a href="#">AOZ1041AI</a>     | <a href="#">AOZ1044PI</a>     |
| <a href="#">AOZ1046AI</a>      | <a href="#">AOZ1051PI</a>     | <a href="#">AOZ1053PI</a>     | <a href="#">AOZ1056AIL</a>    | <a href="#">AOZ1057AI</a>     |
| <a href="#">AOZ1068DI</a>      | <a href="#">AOZ1070AI</a>     | <a href="#">AOZ1071AI</a>     | <a href="#">AOZ1072AI</a>     | <a href="#">AOZ1072AI3</a>    |
| <a href="#">AOZ1073AI</a>      | <a href="#">AOZ1073AI3</a>    | <a href="#">AOZ1073AIL</a>    | <a href="#">AOZ1073AIL-04</a> | <a href="#">AOZ1073AIL-3</a>  |
| <a href="#">AOZ1073AIL-3_2</a> | <a href="#">AOZ1075AI</a>     | <a href="#">AOZ1076PI</a>     | <a href="#">AOZ1079PI</a>     | <a href="#">AOZ1081AI</a>     |
| <a href="#">AOZ1094AI</a>      | <a href="#">AOZ1094AIL</a>    | <a href="#">AOZ1094DIL</a>    | <a href="#">AOZ1096PI</a>     | <a href="#">AOZ1117TI-15L</a> |
| <a href="#">AOZ1117TI-18L</a>  | <a href="#">AOZ1117TI-25L</a> | <a href="#">AOZ1117TI-33L</a> | <a href="#">AOZ1117TI-50L</a> | <a href="#">AOZ1117TI-AAL</a> |
| <a href="#">AOZ1120QI</a>      | <a href="#">AOZ1210AI</a>     | <a href="#">AOZ1212AI</a>     | <a href="#">AOZ1212DI</a>     | <a href="#">AOZ1214DI</a>     |
| <a href="#">AOZ1231QI-01</a>   | <a href="#">AOZ1232QI-01</a>  | <a href="#">AOZ1233QI-01</a>  | <a href="#">AOZ1236QI</a>     | <a href="#">AOZ1236QI-02</a>  |
| <a href="#">AOZ1237QI-02</a>   | <a href="#">AOZ1240AI</a>     | <a href="#">AOZ1242DI</a>     | <a href="#">AOZ1253PI</a>     | <a href="#">AOZ1254PI</a>     |

Distributeur de composants électroniques - IC Chips & Fournisseur de modules IGBT.

RFQ Email: [Info@ariat-tech.com](mailto:Info@ariat-tech.com) Site Internet: <https://www.ariat-tech.com>

Avis de droit d'auteur © 1996-2019 ARIAT TECHNOLOGY LIMITED. Tous les droits sont réservés.